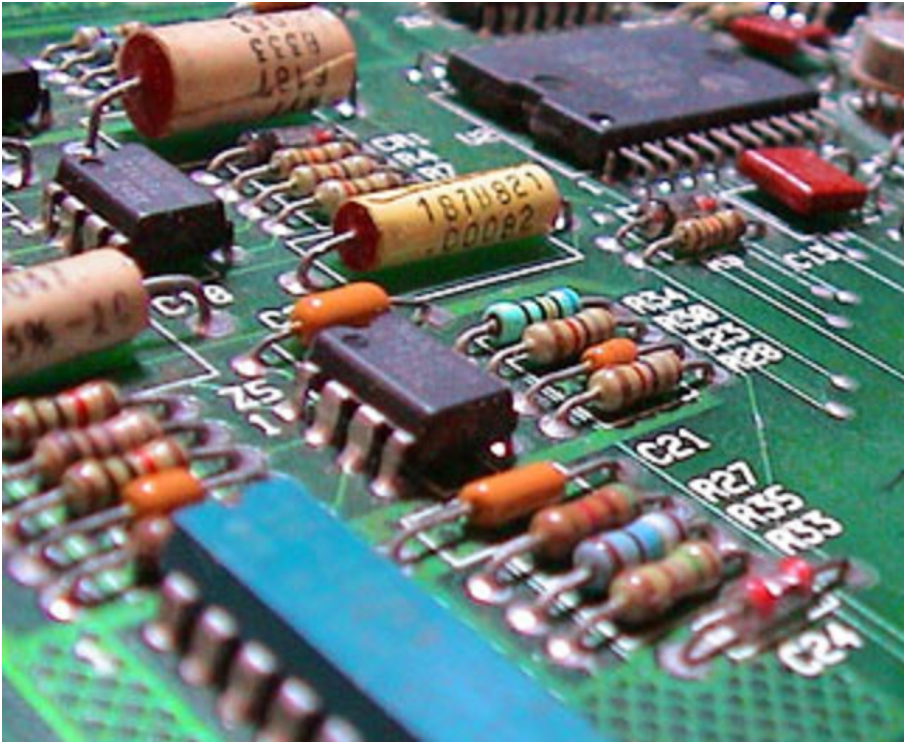


# Electric Circuit Analysis



## TUTORIAL CONTENT

1. The Anatomy of the Cell
2. Network Reductions
3. p.d. and Current Dividers
4. Ohm's, Joule's and intro to Kirchhoff's KCL & KVL\*

G. David Boswell | Chronicles of BÖŞZİK Inc.™

**The 21st Century**



DGB MSE R2S™

# Anatomy of the Cell

---

## Example 01.

The e.m.f. of a cell is  $1.67\text{ V}$ . When it is connected to a  $10\text{-}\Omega$  resistor, its terminal p.d. was measured to be  $1.50\text{V}$ .

Calculate

- (a) the current through the  $10\text{-}\Omega$  external resistor,
- (b) the internal resistance of the cell, and
- (c) the rate of energy loss in the cell (i.e., power loss,  $P_{loss}$  ).




DGB MSE R<sup>2</sup>S™

# Anatomy of the Cell
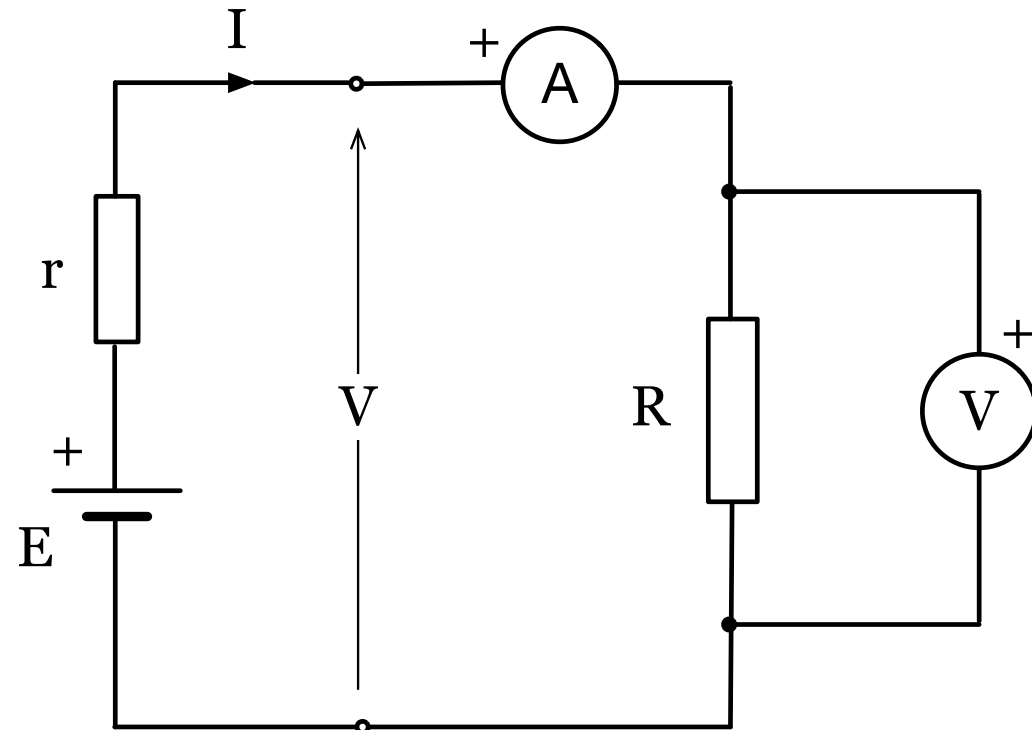
## Response 01.

First, whenever relevant, draw a simplified line diagram that shows problem understanding.

Note very well that when the cell supplies current  $I$  to the load  $R$ , then the e.m.f.,  $E$ , will be greater than the terminal p.d.,  $V$ . In this case,  $E - V = Ir$





DGB MSE R2S™

# Anatomy of the Cell


Terminal p.d.:  
 $V = IR$

## Response 01(a).

*The terminal p.d. is also the voltage across the load resistor,  $R$ ,*

Applying Ohm's Law,
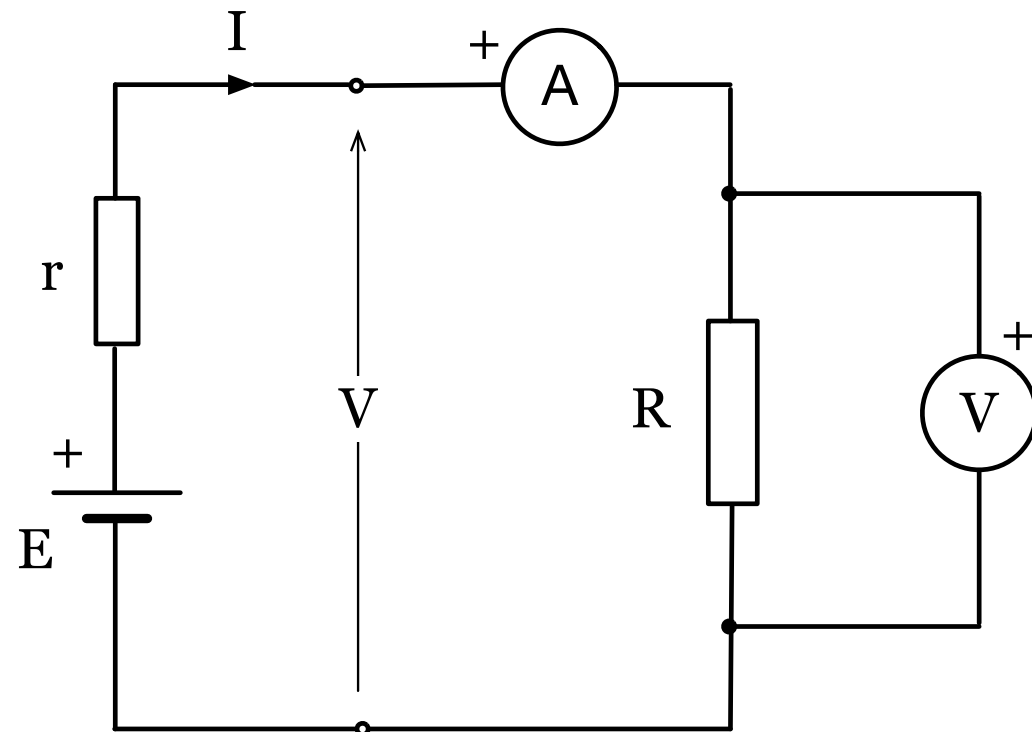
$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{1.50 \text{ V}}{10 \ \Omega} \\ &= \mathbf{0.15 \text{ A}} \end{aligned}$$





DGB MSE R2S™

# Anatomy of the Cell

Cell Model:

$$V = E - Ir$$

## Response 01(b).

Recall that, for a *source*,

$$E - V = Ir$$

Therefore,

$$\begin{aligned} r &= \frac{E - V}{I} \\ &= \frac{(1.67 - 1.50) \text{ V}}{0.15 \text{ A}} \\ &= 1.13 \text{ } \Omega \\ &\approx 1.1 \text{ } \Omega \end{aligned}$$

## Response 01(c).

Due to the internal resistance,

$$\begin{aligned} P_{loss} &= I^2 r \\ &= (0.15 \text{ A})^2 \times 1.13 \text{ } \Omega \\ &\approx 26 \text{ mW} \end{aligned}$$

**Reader** ~ Another approach is:

$$\begin{aligned} P_{loss} &= P_{in} - P_{out} \\ &= EI - VI \\ &= (E - V)I \end{aligned}$$



DGB MSE R2S™

# Anatomy of the Cell

## Example 02.

The terminal p.d. of an interconnections of cells (i.e. a battery) on open-circuit is **100 V**. When it delivers a current of **20.0A** to a circuit, its terminal p.d. falls to **95.4V**.

Calculate

- (a) the efficiency of the battery,  $\eta$ .
- (b) the power output of the battery,  $P_{out}$ .



DGB MSE R2S™

# Anatomy of the Cell

Efficiency:

$$\eta = \frac{V}{E} = \frac{R}{R+r}$$

## Response 02(a).

If  $P_{in}$  is the input power conversion to electrical inside the battery, and  $P_{out}$  is the output power conversion at the terminals of the battery, then the efficiency of the battery is

$$\begin{aligned}\eta &= \frac{P_{out}}{P_{in}} \times 100\% \\ &= \frac{V}{E} \times 100\% \quad \text{since } P_{out} = VI \quad \text{and } P_{in} = EI \\ &= \frac{95.4}{100} \times 100\% \\ &= 95.4 \%\end{aligned}$$



DGB MSE R2S™

# Anatomy of the Cell

Output Power

$$P_{out} = VI = \eta EI$$

## Response 02(b).

$P_{out}$  is the output power conversion from electrical to other forms realized at the terminals of the battery.

For this problem,

$$\begin{aligned} P_{out} &= VI \\ &= 95.4 \text{ V} \times 20.0 \text{ A} \\ &= 1,890 \text{ W} \\ &= \mathbf{1.89 \text{ kW}} \end{aligned}$$






# Network Reduction

## Example 03.

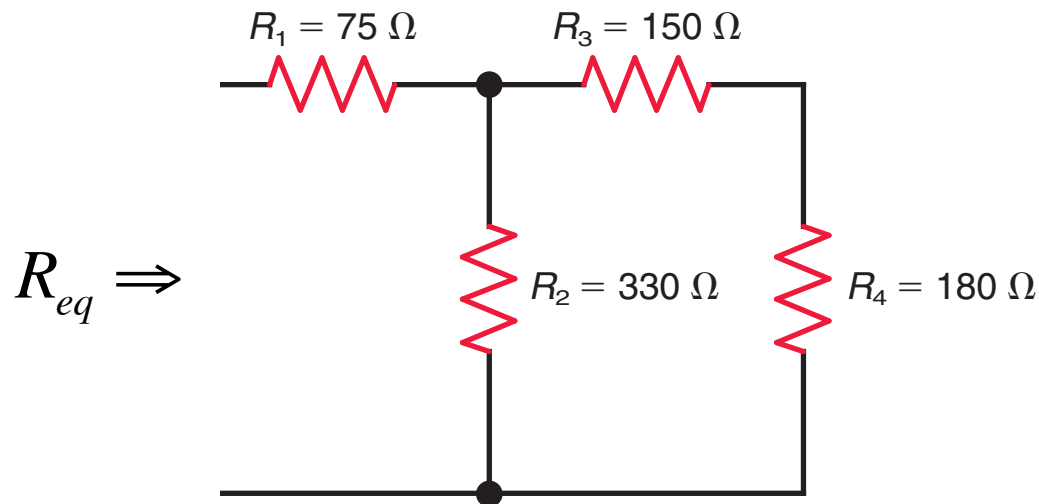- (a) Find  $R_{eq}$ , the equivalent resistance of the network shown.
- (b) Repeat (a) when.  $R_4 = 0\Omega$  (i.e., an ideal short circuit)
- (c) Repeat (a) when  $R_4 \rightarrow \infty$  (i.e., a practical open circuit)





DGB MSE R2S™

# Network Reduction

Series:

$$R_S = \sum_{i=1}^n R_i$$

## Response 03(a).

Using the formulations for resistors in series and parallel,

$$R_{eq} = R_1 + \frac{R_2 (R_3 + R_4)}{R_2 + (R_3 + R_4)} \quad \text{"product over sum"}$$

$$= R_1 + \frac{R_2}{2} \quad \text{since, in this case, } R_2 = R_3 + R_4$$

$$= 75\Omega + 165\Omega$$

$$= \mathbf{240\Omega}$$

NB: (a) For n equal resistors in series:  $R_S = nR$

(b) For n equal resistors in parallel:  $R_P = \frac{R}{n}$



DGB MSE R2S™

# Network Reduction

Parallel:


$$R_P = \left( \sum_{i=1}^n R_i \right)^{-1}$$

## Response 03(b).

When  $R_4$  is “shorted,” then

$$\begin{aligned} R_{eq} &= R_1 + \frac{R_2 R_3}{R_2 + R_3} \\ &= 75\Omega + \left( \frac{330 \times 150}{330 + 150} \right) \Omega \\ &= 178.1\Omega \end{aligned}$$

$R_{eq} \Rightarrow$

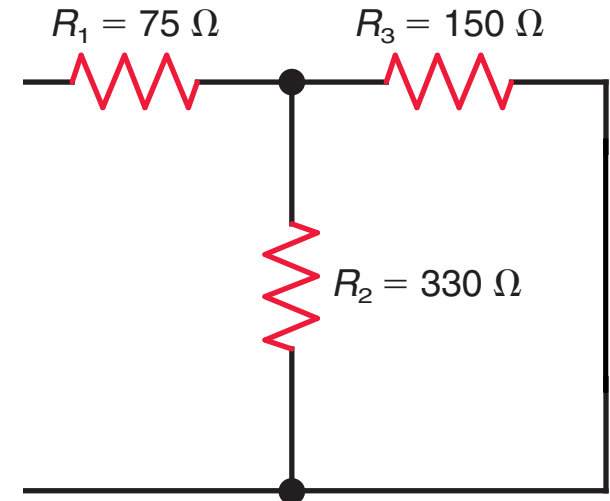

NB: For 2 resistors in parallel, we utilize

“product over sum”:  $R_a // R_b = \frac{R_a R_b}{R_a + R_b}$




DGB MSE R<sup>2</sup>S™

# Network Reduction
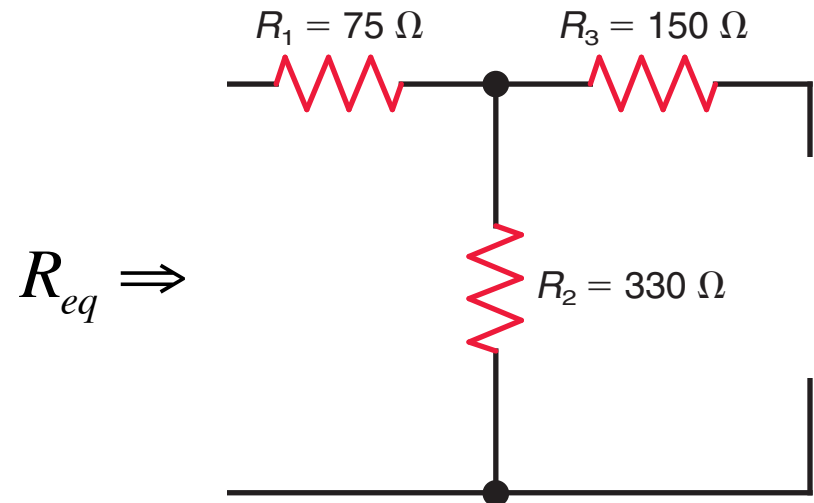
## Response 03(c).

When  $R_4$  is “opened,” then because its loop is broken,  $R_1$  and  $R_2$  are now in series such that

$$\begin{aligned} R_{eq} &= R_1 + R_2 \\ &= 75\Omega + 330\Omega \\ &= 405\Omega \end{aligned}$$






DGB MSE R<sup>2</sup>S™

# Potential Divider

## Example 04.

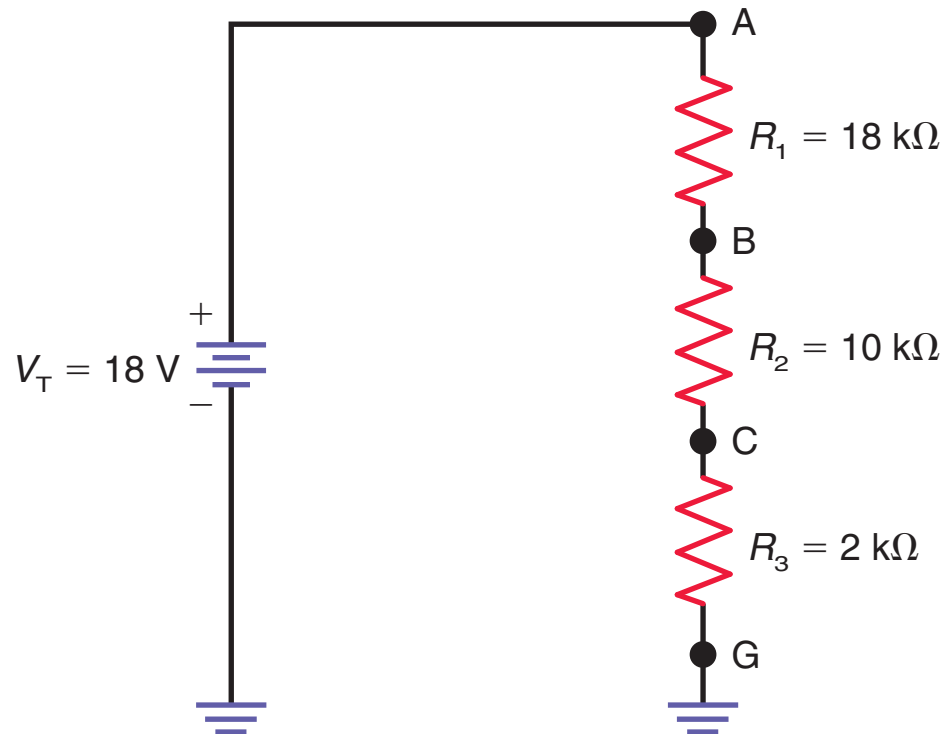- (a) Find  $R_T$ , the total resistance of the network shown.
- (b) Compute the p.d. across each resistor.






DGB MSE R2S™

# Potential Divider
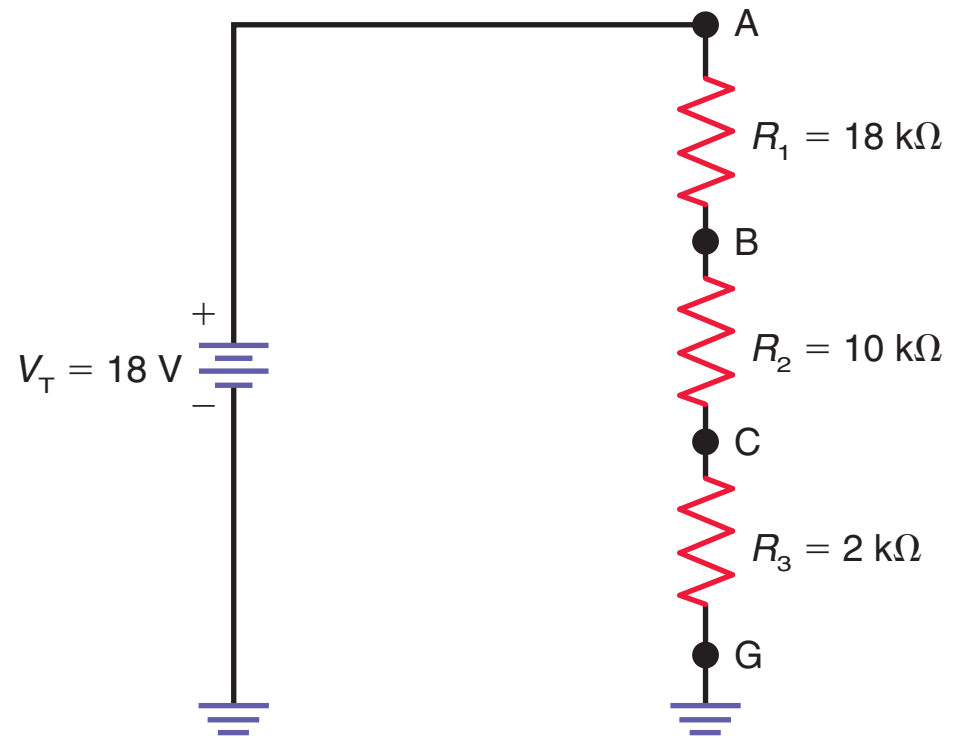
## Response 04(a).

Using the formulation for combining 3 resistors in series,

$$\begin{aligned} R_T &= \sum_{i=1}^3 R_i \\ &= R_1 + R_2 + R_3 \\ &= 18\Omega + 10\Omega + 2\Omega \\ &= 30 \Omega \end{aligned}$$





# Potential Divider

$$V_i = \frac{R_i}{R_S} V$$

## Response 04(b).

The p.d. across each resistor in the series network is

$$\begin{aligned} V_1 &= \frac{R_1}{R_T} V_T \\ &= \frac{18\Omega}{30\Omega} \times 18V \\ &= 10.8 V \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{R_2}{R_T} V_T \\ &= \frac{10\Omega}{30\Omega} \times 18V \\ &= 6.0 V \end{aligned}$$

$$\begin{aligned} V_3 &= \frac{R_3}{R_T} V_T \\ &= \frac{2\Omega}{30\Omega} \times 18V \\ &= 1.2 V \end{aligned}$$

Note that, in accordance with KVL:  $V_T = \sum_{i=1}^n V_i$




DGB MSE R<sup>2</sup>S™

# Potential Divider
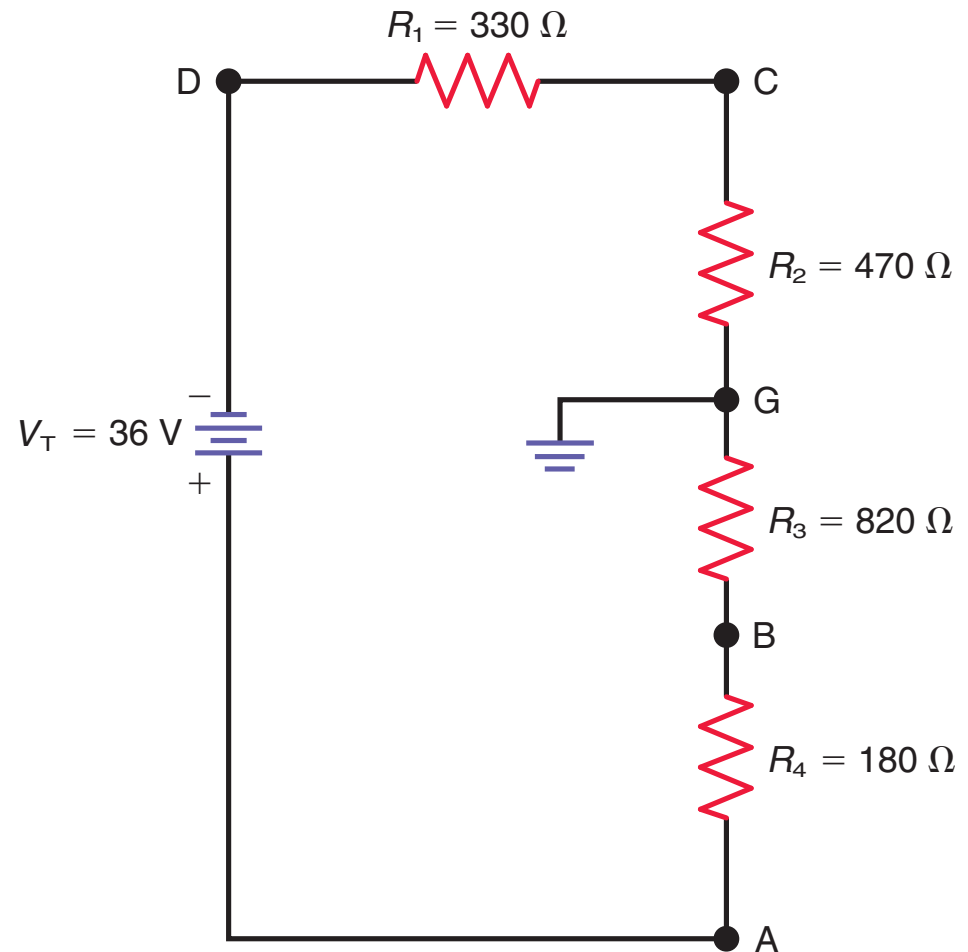
## Example 05.

- Find  $R_T$ , the total resistance of the network shown.
- Compute the p.d. across each resistor.
- Hence, calculate the  $V_C$  and  $V_B$ , the potentials at nodes **C** and **B**, respectively.







DGB MSE R2S™

# Potential Divider

## Response 05(a).

Using the formulation for combining 4 resistors in series, we get

$$\begin{aligned}R_T &= \sum_{i=1}^4 R_i \\&= R_1 + R_2 + \dots + R_4 \\&= 330 + 470 + 820 + 180 \quad \Omega \\&= 1,800 \quad \Omega \\&= 1.80 \text{ k}\Omega\end{aligned}$$



DGB MSE R2S™

# Potential Divider

## Response 05(b).

The respective p.d. across the first 2 resistors in the network is

$$\begin{aligned} V_1 &= \frac{R_1}{R_T} V_T \\ &= \frac{330\Omega}{1,800\Omega} \times 36V \\ &= 6.6 V \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{R_2}{R_T} V_T \\ &= \frac{470\Omega}{1,800\Omega} \times 36V \\ &= 9.4 V \end{aligned}$$



DGB MSE R<sup>2</sup>S™

# Potential Divider

## Response 05(b). (cont.d)

Similarly, for the other 2 resistors in the series circuit,

$$\begin{aligned}V_3 &= \frac{R_3}{R_T} V_T \\ &= \frac{820\Omega}{1,800\Omega} \times 36V \\ &= 16.4 V\end{aligned}$$

$$\begin{aligned}V_4 &= \frac{R_4}{R_T} V_T \\ &= \frac{180\Omega}{1,800\Omega} \times 36V \\ &= 3.6 V\end{aligned}$$

Note that, in accordance with KVL:  $V_T - \sum_{i=1}^n V_i = 0$  volts



DGB MSE R2S™

# Potential Divider

## Response 05(c).


The reference p.d. is  $V_G = 0V$ .

And, based on battery polarity,

$$\begin{aligned} V_C &= V_G - V_2 \\ &= 0V - 9.4V \\ &= -9.4V \end{aligned}$$

$$\begin{aligned} V_B &= V_G + V_3 \\ &= 0V + 16.4V \\ &= 16.4V \end{aligned}$$

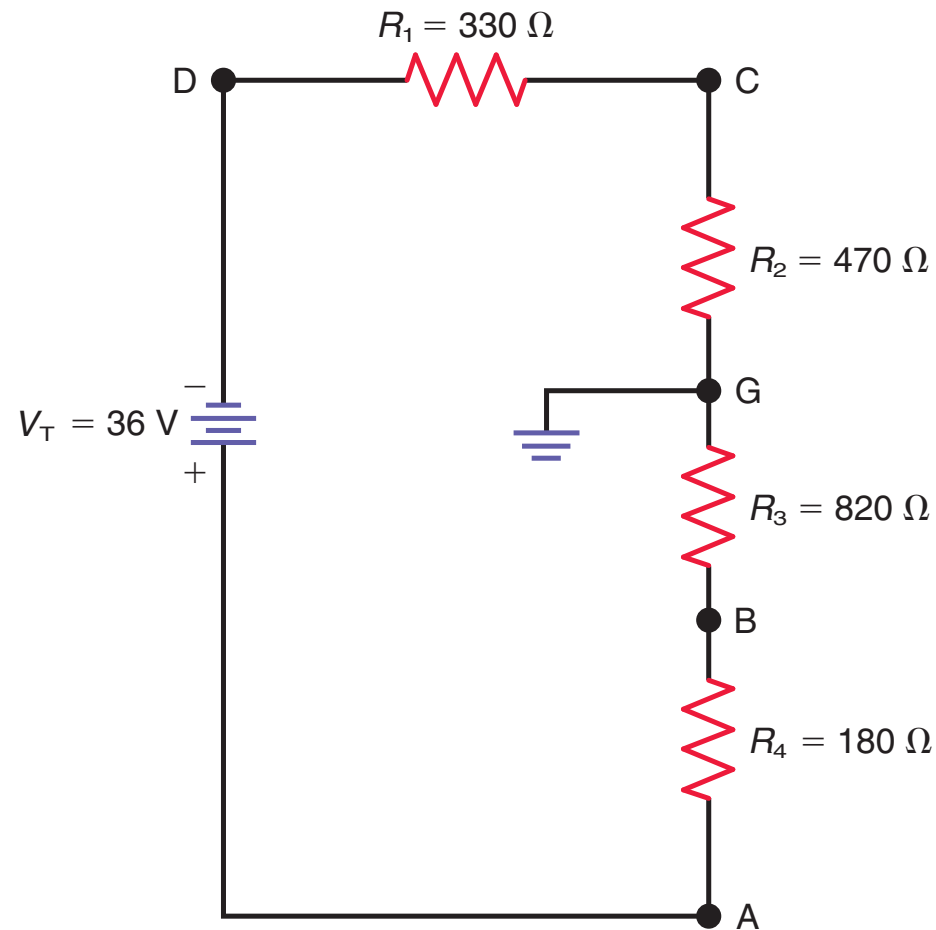*The lowest voltage potential is at node D and the highest voltage potential is at node A.*






# Current Divider

## Example 06.

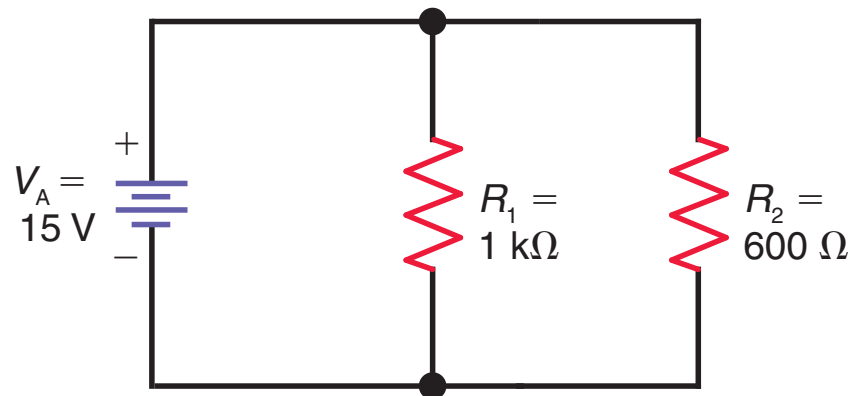- (a) Find  $R_T$ , the total resistance of the network shown.
- (b) Calculate the total current in the circuit.
- (c) Compute the current through each resistor and verify that Kirchhoff's Current Law (KCL) holds true.





DGB MSE R2S™

# Current Divider

## Response 06(a).

Using the formulation for combining 2 resistors in parallel, we get

$$\begin{aligned} R_T &= \left( \frac{1}{R_1} + \frac{1}{R_{12}} \right)^{-1} \\ &\equiv \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{1000 \times 600}{1000 + 600} \quad \Omega \quad (\text{all values in the same units!}) \\ &= \mathbf{375 \, \Omega} \end{aligned}$$



DGB MSE R2S™

# Current Divider

## Response 06(b).

Using Ohm's Law, the total current in the circuit is

$$\begin{aligned} I_T &= \frac{V_A}{R_T} \\ &= \frac{15V}{375\Omega} \\ &= 0.040A \\ &= 40 \text{ mA} \end{aligned}$$



DGB MSE R2S™

# Current Divider

## Response 06(c).

Using the Current Divider formulation, then the current in the respective parallel branches are

$$\begin{aligned} I_1 &= \left( \frac{R_2}{R_1 + R_2} \right) I_T \\ &= \frac{600\Omega}{1600\Omega} \times 40\text{mA} \\ &= 15\text{ mA} \end{aligned}$$

$$\begin{aligned} I_2 &= \left( \frac{R_1}{R_1 + R_2} \right) I_T \\ &= \frac{1000\Omega}{1600\Omega} \times 40\text{mA} \\ &= 25\text{ mA} \end{aligned}$$






# Current Divider
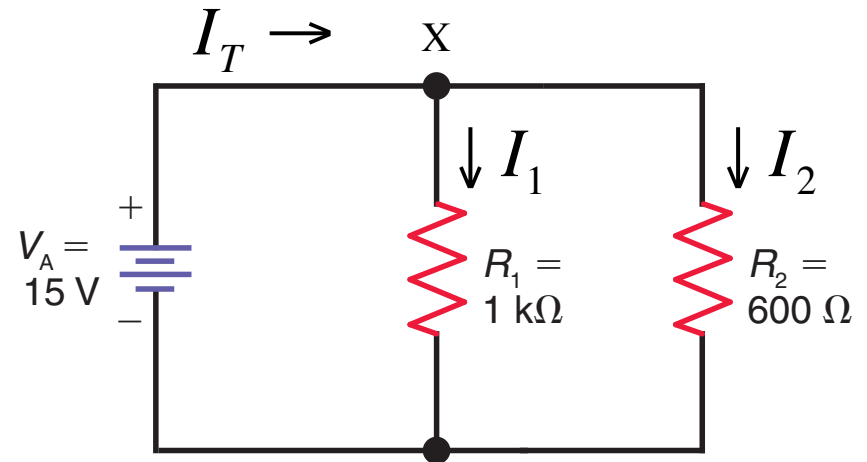
## Response 06(c). (cont.d)

Now, the algebraic sum of the currents at node X in the circuit is

$$\begin{aligned} \sum_{\text{At Node X}} I &= I_1 + I_2 - I_T \\ &= (15 + 25 - 40) \text{ mA} \\ &= 0 \end{aligned}$$



Therefore, KCL is verified.




DGB MSE R2S™

# Current Divider

## Example 07.

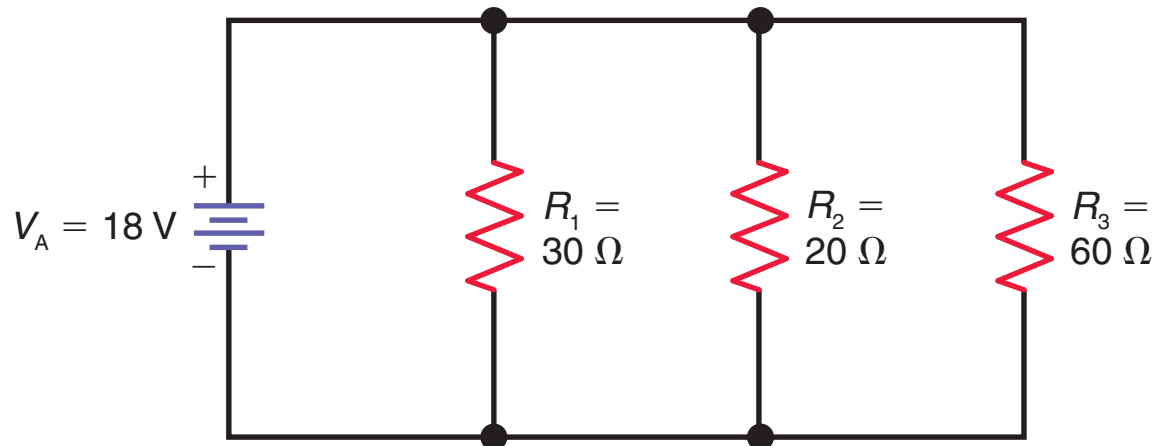- (a) Find  $R_T$ , the total resistance of the network shown.
- (b) Compute the total current from the 18V source.
- (c) Compute the current through each each resistor.





DGB MSE R2S™

# Current Divider


Parallel:

$$R_P = \left( \sum_{i=1}^n \frac{1}{R_i} \right)^{-1}$$
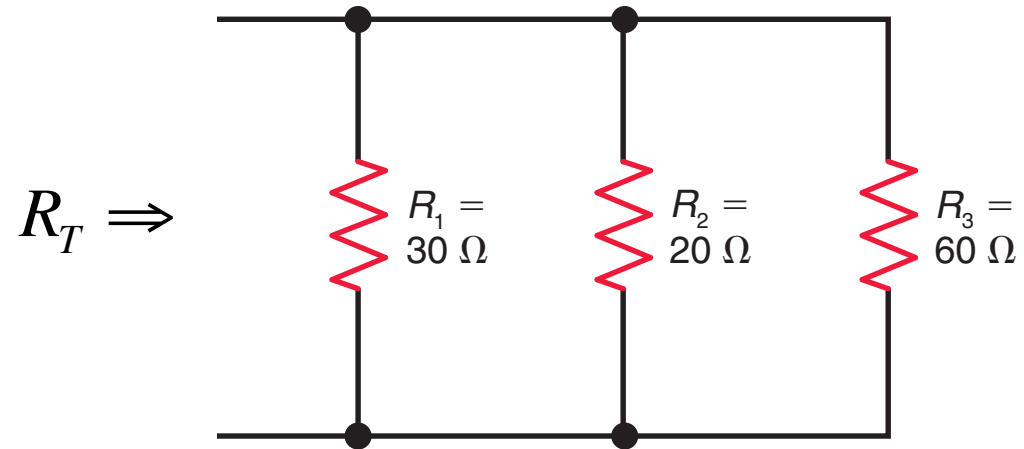
## Response 07(a).

The total resistance of the parallel network is

$$\begin{aligned} R_T &= \left( \sum_{i=1}^3 \frac{1}{R_i} \right)^{-1} \\ &= \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \\ &= \left( \frac{1}{30} + \frac{1}{20} + \frac{1}{60} \right)^{-1} \Omega \\ &= 10 \Omega \end{aligned}$$





DGB MSE R2S™

# Current Divider


Parallel:

$$R_P = \left( \sum_{i=1}^n \frac{1}{R_i} \right)^{-1}$$
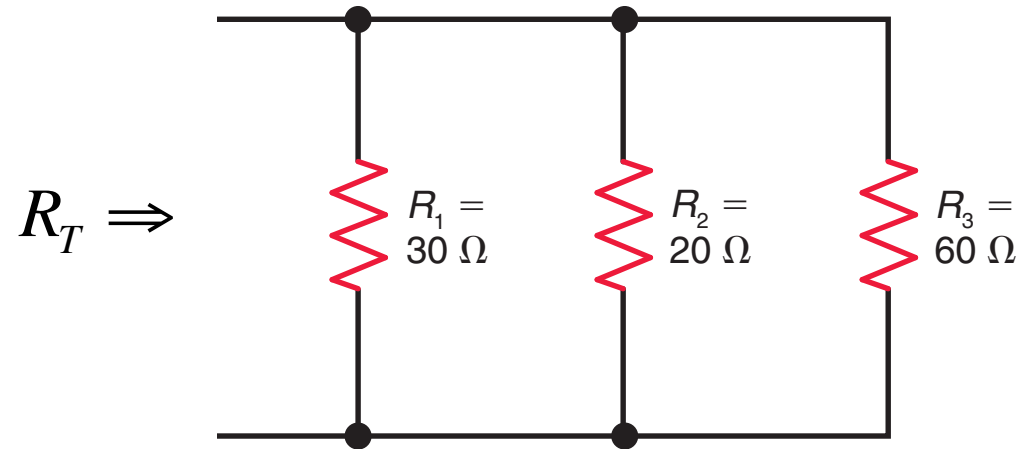
## Response 07(b).

The total current delivered by the source is

$$\begin{aligned} I_T &= \frac{V_A}{R_T} \\ &= \frac{18V}{10\Omega} \\ &= 1.8 \text{ A} \end{aligned}$$





DGB MSE R2S™

# Current Divider

## Response 07(c).

Since all 3 resistors are in parallel with the source, then:

$$\begin{aligned} I_1 &= \frac{V_A}{R_1} \\ &= \frac{18 \text{ V}}{30 \ \Omega} \\ &= \mathbf{0.6 \text{ A}} \end{aligned}$$

$$\begin{aligned} I_2 &= \frac{V_A}{R_2} \\ &= \frac{18 \text{ V}}{20 \ \Omega} \\ &= \mathbf{0.9 \text{ A}} \end{aligned}$$

$$\begin{aligned} I_3 &= \frac{V_A}{R_3} \\ &= \frac{18 \text{ V}}{60 \ \Omega} \\ &= \mathbf{0.3 \text{ A}} \end{aligned}$$

Reader: Using these results, please verify KCL:

$$\sum_{\text{at node}} I = 0 \text{ A}$$




DGB MSE R2S™

# Network Analysis

## Example 08.

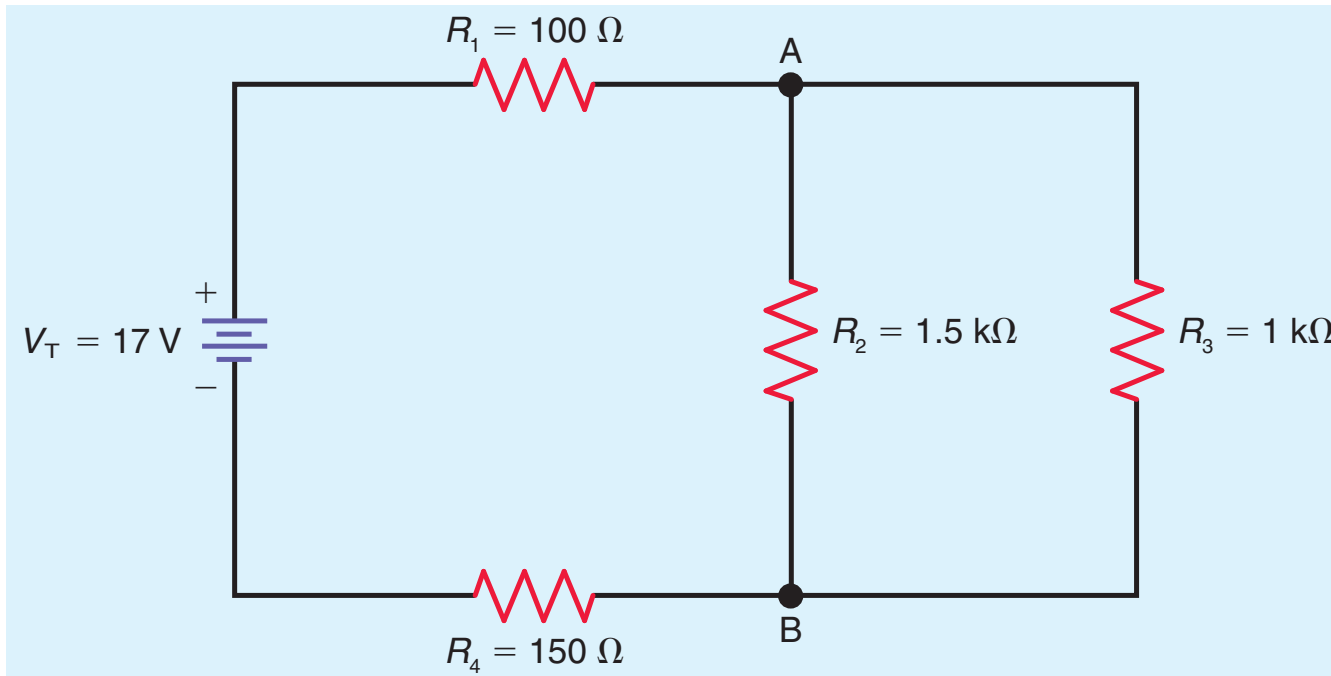- (a) Find  $R_{eq}$ , the total resistance of the network shown.
- (b) Compute  $V_{AB}$  and the power loss in  $R_3$ .





DGB MSE R<sup>2</sup>S™

# Network Analysis

## Response 08(a).

Using the formulations for resistors in series and parallel,

$$\begin{aligned}R_{eq} &= R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4 \\&= 100\Omega + \left(\frac{1.5 \times 1}{1.5 + 1}\right) k\Omega + 150\Omega \\&= 250\Omega + 600\Omega \\&= 850 \Omega\end{aligned}$$

NB: (a) For 2 resistors in parallel, “product over sum” is quickly used.

(b) Please pay attention the mixed units and the final conversions!




DGB MSE R2S™

# Network Analysis
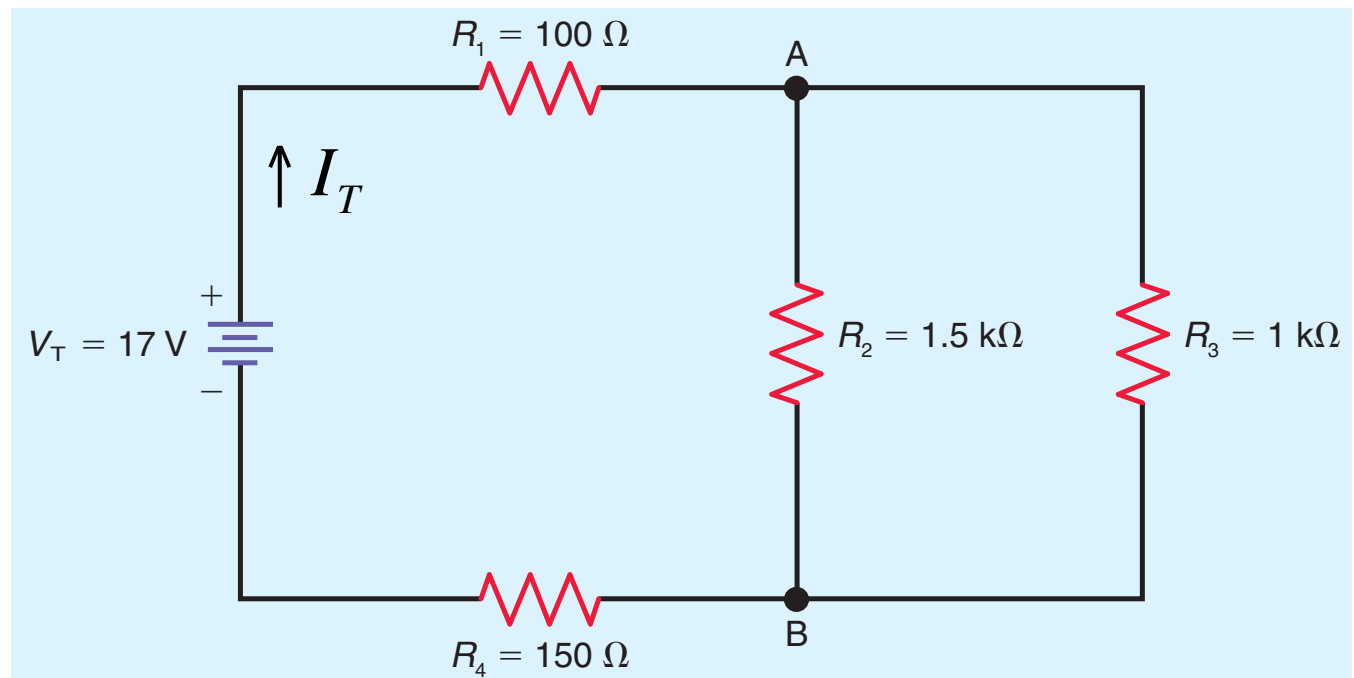
## Response 08(b).

First, find the total current delivered by the source is

$$\begin{aligned} I_T &= \frac{V_T}{R_{eq}} \\ &= \frac{17V}{850\Omega} \\ &= 20 \text{ mA} \end{aligned}$$







DGB MSE R<sup>2</sup>S™

# Network Analysis

## Response 08(b). (cont.d)

Now, the total voltage drop across  $R_1$  &  $R_4$ , which are in series, is

$$\begin{aligned}\Delta V &= I_T (R_1 + R_4) \\ &= 20mA \times (100 + 150) \Omega \\ &= 5V\end{aligned}$$

So, the required p.d. across nodes A and B is

$$\begin{aligned}V_{AB} &= V_T - \Delta V \\ &= 17V - 5V \\ &= 12 V\end{aligned}$$



DGB MSE R<sup>2</sup>S™

# Network Analysis

## Response 08(b). (cont.d)

And, finally, power loss in  $R_3$  is

$$P_3 = \frac{V_{AB}^2}{R_3} \quad (\text{Joule's Law})$$

$$= \frac{(12V)^2}{k\Omega}$$

$$= 144 \times 10^{-3} W$$

$$= 144 \text{ mW}$$

# R2S Legacy Tutorial 03

## Electric Circuit Analysis

---





DGB MSE R2S™

# Anatomy of the Cell



## Question 01.

The e.m.f. of a cell is  $10.7 \text{ V}$ . When it is connected to a  $12.0\text{-}\Omega$  load resistor, the terminal p.d. drooped by  $10.0\%$ . Calculate

- (a) the terminal p.d. of the cell,  $V$ .
- (b) the load current  $I$ .
- (c) the internal resistance of the cell,  $r$ .
- (d) the rate of energy loss in the cell (i.e., power loss,  $P_{loss}$  )
- (e) the *fractional efficiency* of the cell.




# Network Reduction



## Question 02.

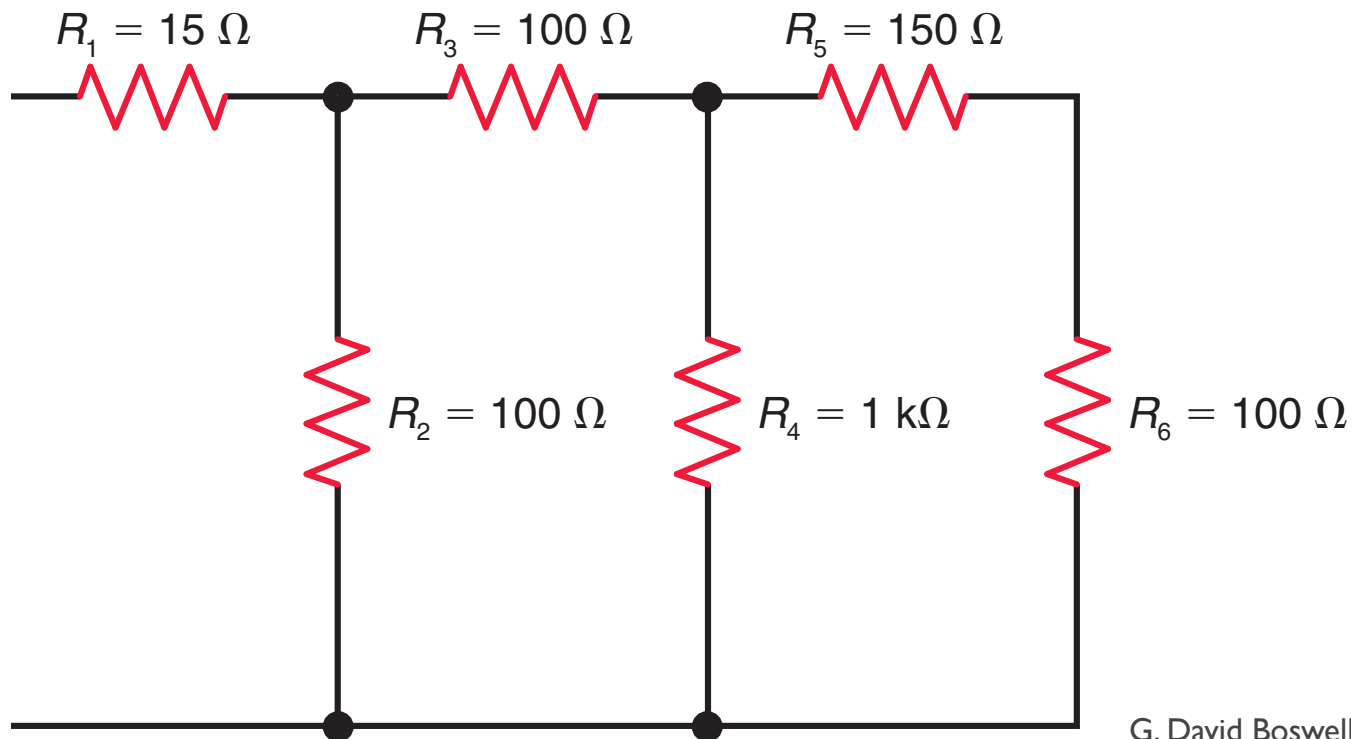- (a) Find  $R_{eq}$ , the equivalent resistance of the network shown.
- (b) Repeat (a) when  $R_3 = 0$  and  $R_4 \rightarrow \infty$  simultaneously.






# Potential Divider



## Question 03.

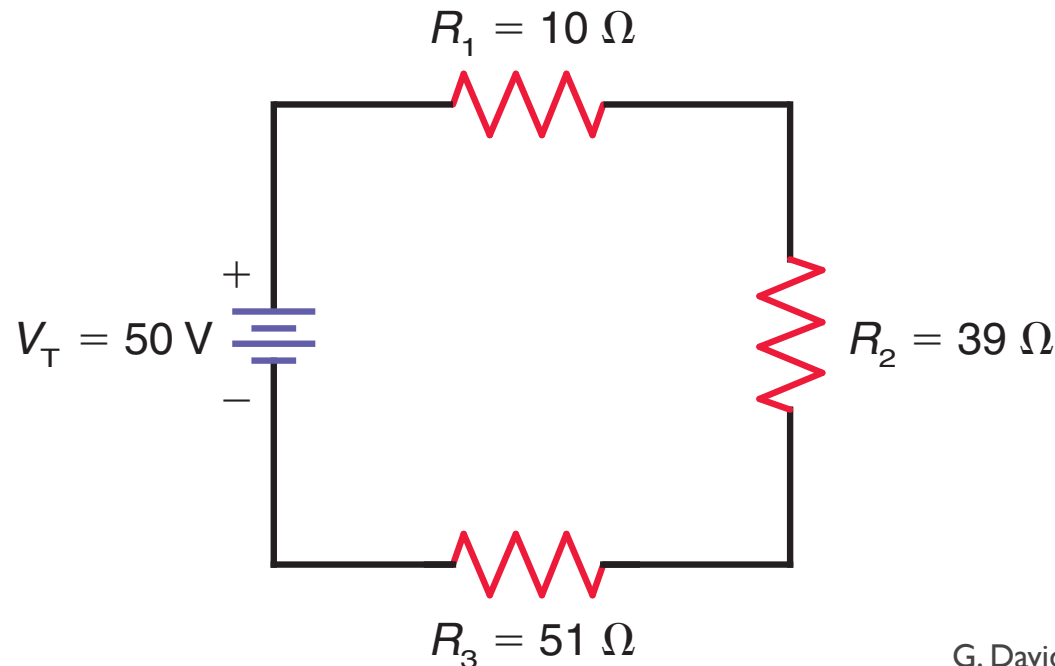- (a) Find  $R_T$ , the total resistance of the network shown.
- (b) Compute,  $V_1$ ,  $V_2$  and  $V_3$ , the respective voltage drops across each resistor.






# Potential Divider



## Question 04.

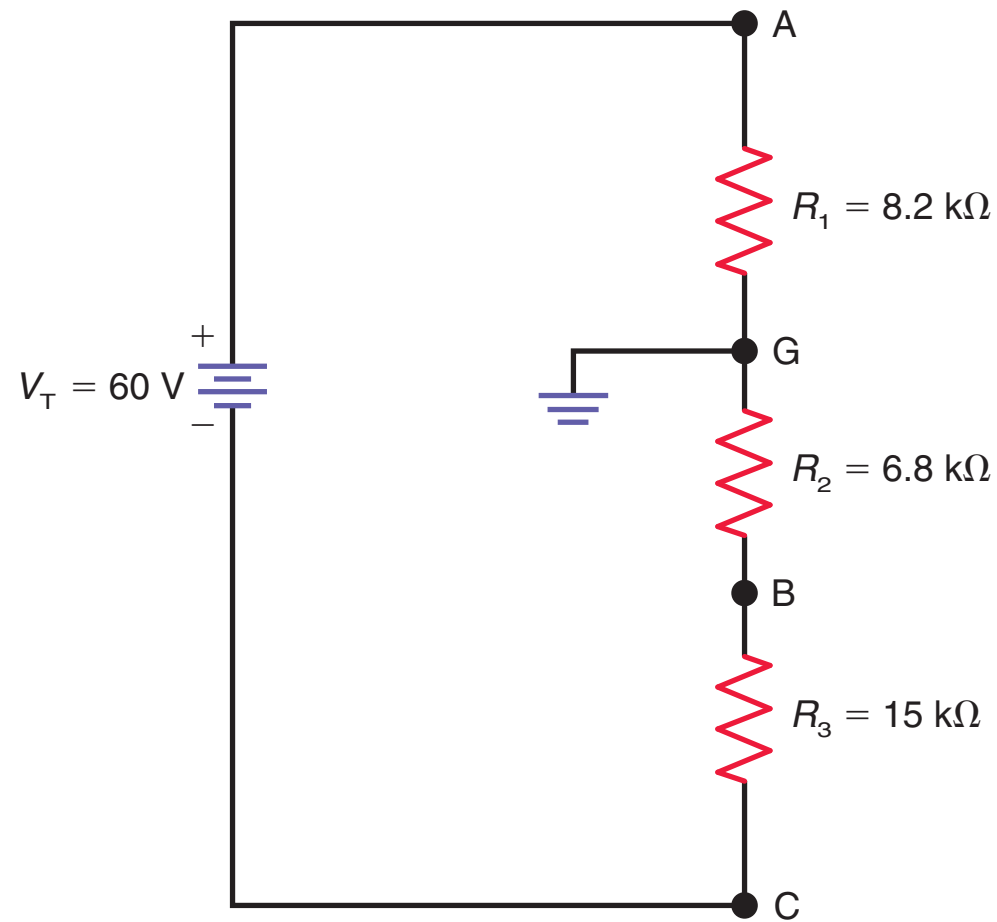- (a) Find  $R_S$ , the total resistance of the network shown.
- (b) Compute the p.d. across each resistor.
- (c) Hence, calculate the  $V_C$  and  $V_B$ , the potentials at nodes **C** and **B**, respectively.






# Current Divider



## Question 05.

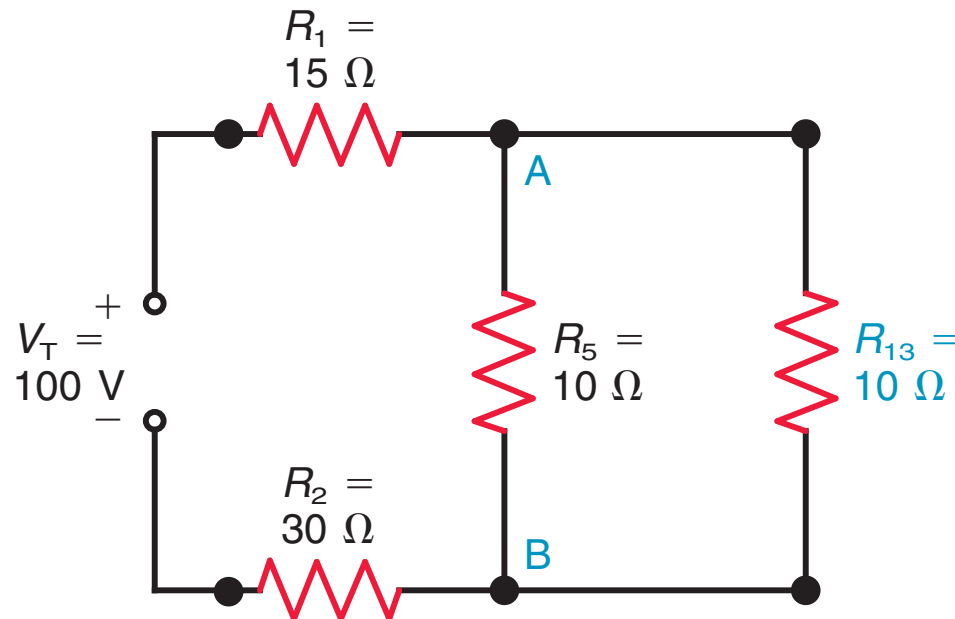- (a) Find  $R_T$ , the total resistance of the network shown.
- (b) Hence, compute the total current supplied and also the current through each each of the 4 resistors.








# Current Divider



## Question 06.

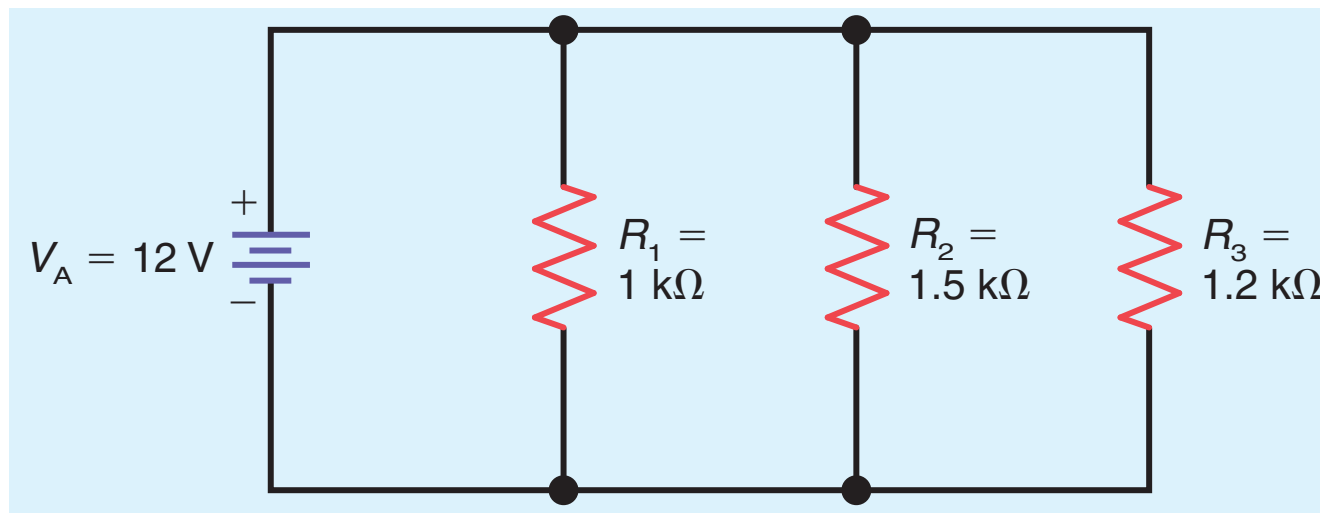- (a) Find  $R_p$ , the total resistance of the network shown.
- (b) Compute the current supplied by the source voltage.
- (c) Compute the current through each resistor and verify the Kirchhoff's Current Law (KCL) holds true.







# Network Analysis



## Question 07.

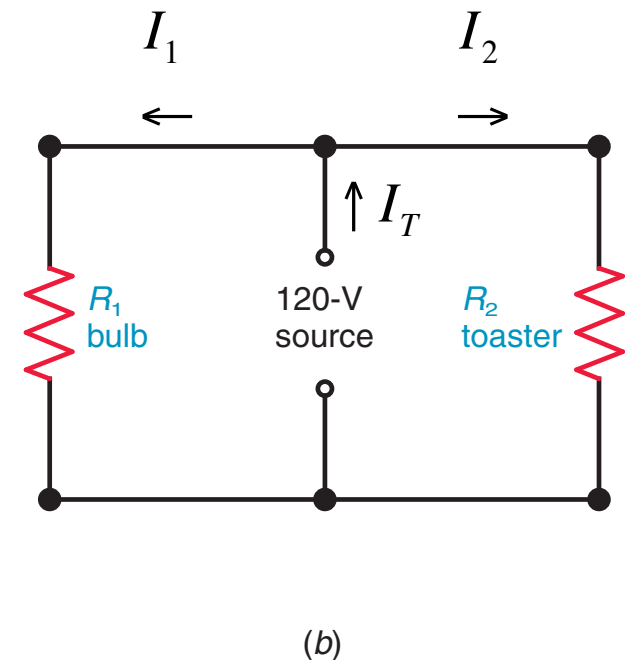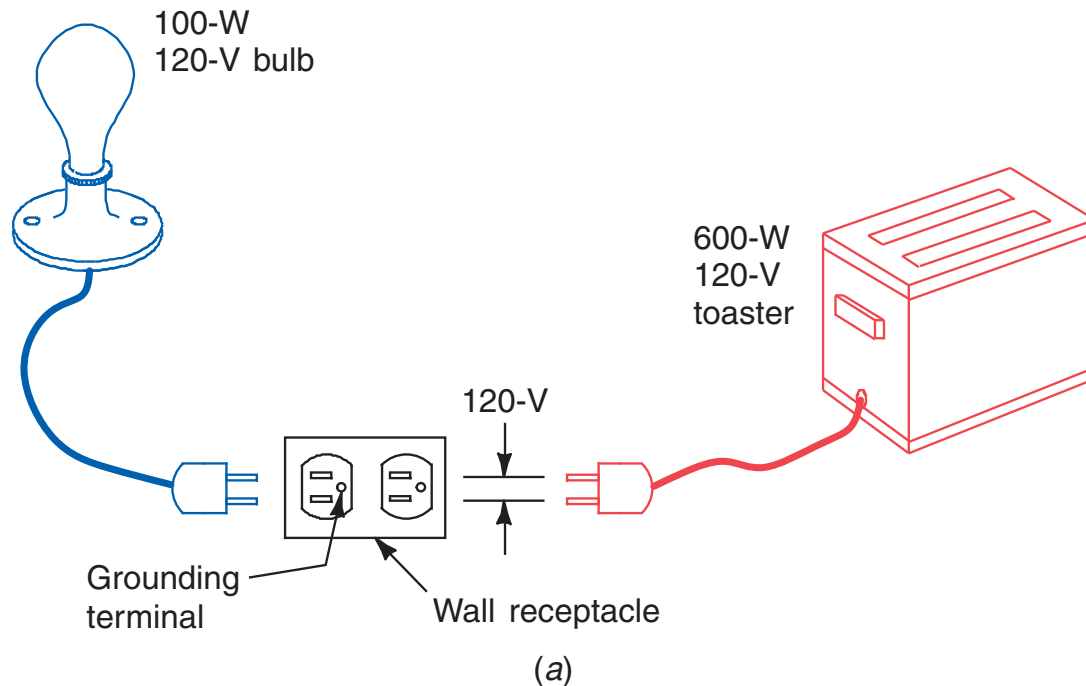- (a) Find resistances  $R_1$  and  $R_2$  using Ohm's and Joule's Law.
- (b) Use "Current Division" and Ohm's Law to find  $I_1$  and  $I_2$ .






# Network Analysis



## Question 08.

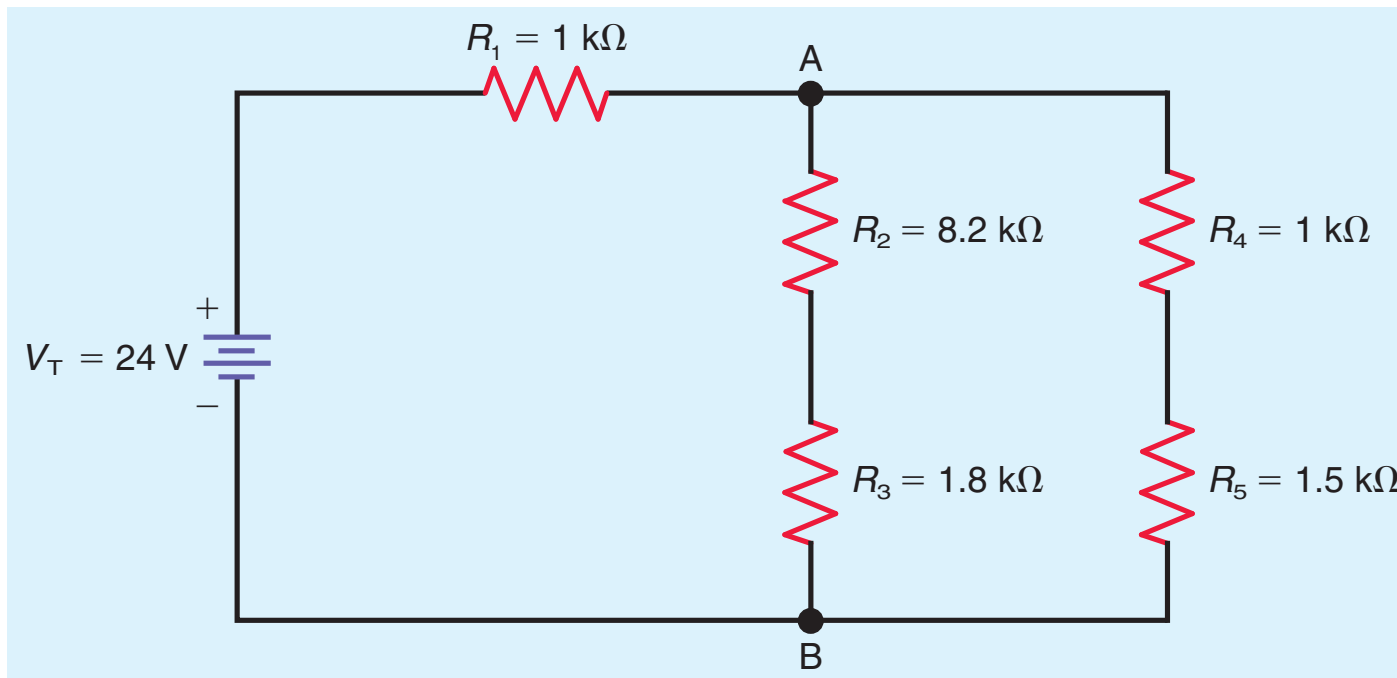- (a) Find  $R_{eq}$ , the total resistance of the network shown.
- (b) Compute  $V_{AB}$  and the power losses in  $R_1$  and  $R_5$ .



# R2S Legacy Tutorial 04

## Mesh and Nodal Analyses

---



10.12.21 ... High Noon\*

# Electric Circuit Analysis

Thank You

© BÖ&ZiK Inc.™

All Publication Rights Reserved

For more information, please visit:

<http://www.boszik.net/projects>